

- 1) An electric circuit consists only of a charged capacitor ($C=3.3\mu\text{F}$) and an inductor ($L=0.3\mu\text{H}$).
- Draw a corresponding circuit diagram.
 - What is the frequency of the oscillating B- and E-fields?